
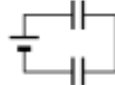


Chapter 26 Even Answers

2. (a) $1.00 \mu\text{F}$ (b) 100 V
4. (a) 8.99 mm (b) 0.222 pF (c) $2.22 \times 10^{-11} \text{ C}$
6. $11.1 \text{ nF}, 26.6 \text{ C}$
8. 3.10 nm
10. $\frac{(2N-1)(\pi-\theta)R^2\epsilon_0}{d}$
12. $2.13 \times 10^{16} \text{ m}^3$
14. $\frac{mgd \tan \theta}{q}$
16. $708 \mu\text{F}$
18. (a) $3.53 \mu\text{F}$ (b) 6.35 V and 2.65 V (c) $31.8 \mu\text{C}$ on each
20. $\frac{1}{2}C_p \pm \sqrt{\frac{1}{4}C_p^2 - C_p C_s}$
22. $C_{eq} = 1.83C$
24. (a) $398 \mu\text{F}$ in series (b) $2.20 \mu\text{F}$ in parallel
26. $\frac{60R}{37k_e}$
28. $6.04 \mu\text{F}$
30. $12.9 \mu\text{F}$
32. (a) Circuit diagram:

 Stored energy = 0.150 J
- (b) Potential Difference = 268 V
 Circuit Diagram:

34. $2.51 \times 10^{-3} \text{ m}^3, 2.51 \text{ L}$
36. $\frac{Q^2}{2A\epsilon_0 k}$
40. 10.8 pF

42. (a) 13.3 nC (b) 272 nC
44. $\sim 10^{-6}$ F and $\sim 10^2$ V for two 40-cm by 100-cm sheets of aluminum foil sandwiching a thin sheet of plastic.
46. (a) 369 pC (b) 118 pF, 3.12 V (c) -45.5 nJ
48. (a) 1.53 nF (b) 18.4 nC
(c) 1.84×10^{-4} C/m², 1.83×10^{-4} C/m² (d) 694 V/m
50. (a) $(-9.10\mathbf{i} + 8.40\mathbf{j}) \times 10^{-12}$ C·m (b) $(-2.09 \times 10^{-8} \mathbf{k})$ N·m
(c) 112 nJ (d) 228 nJ
52. 579 V
54. (a) 3.33 μ F (b) 60.0 V, 30.0 V, 60.0 V, 30.0 V
(c) 180 μ C, 180 μ C, 120 μ C, 120 μ C (d) 13.4 mJ
56. (a) 4.00×10^{-5} J (b) 500 V
58. (a) $\frac{\epsilon_0 A}{d} \left(\frac{\kappa_1}{2} + \frac{\kappa_2 \kappa_3}{\kappa_2 + \kappa_3} \right)$ (b) 1.76 pF
60. (b) $\frac{1}{C} \rightarrow \frac{1}{4\pi\epsilon_0 a} + \frac{1}{4\pi\epsilon_0 b}$
62. (a) $\frac{\epsilon_0}{d} (1^2 + 1x(\kappa - 1))$ (b) $\frac{\epsilon_0 (\Delta V)^2}{2d} (1^2 + 1x(\kappa - 1))$
(c) $\frac{\epsilon_0 (\Delta V)^2}{2d} 1(\kappa - 1)$ to the left (d) 1.55×10^{-3} N
64. Gasoline has 194 times the specific energy content of the battery and 727000 times that of the capacitor.
66. Put five 6.00 pF capacitors in series.
68. 8.00 kV
70. (a) $\frac{\kappa_1 \kappa_2 \epsilon_0 W L}{(\kappa_1 - \kappa_2) d} \ln \left(\frac{\kappa_1}{\kappa_2} \right)$
72. 750 μ C on C_1 , 250 μ C on C_2
76. $\frac{4}{3} C$

