

Chapter 32 Even Answers

2. $1.36 \mu\text{H}$
4. 7.80×10^3 turns / m
6. 2.37 mV
8. $19.2 \mu\text{T} \cdot \text{m}^2$
10. $-\frac{El}{\mu_0 N^2 A}$
12. (a) $188 \mu\text{T}$ (b) $3.33 \times 10^{-8} \text{T} \cdot \text{m}^2$ (c) 0.375 mH
(d) B and Φ_B are proportional to current; L is independent of current.
16. 1.92Ω
20. 92.8 V
22. 30.0 mH
24. 7.67 mH
26. (a) 1.00 k Ω (b) 3.00 ms
28. (a) 1.00 A (b) 12.0 V, 1.20 kV, 1.21 kV (c) 7.62 ms
30. (a) See solution (b) See solution
(c) See solution (d) Yes. See solution.
32. (a) 8.06×10^6 J / m³ (b) 6.32 kJ
34. (a) 27.8 J (b) 18.5 ms
36. (a) 0.500 J (b) 4.00 W (c) 11.0 W
38. 2.27×10^{-3} T
40. 1.73 mH
42. 80.0 mH
44. 138 nH
46. 781 pH

48. 0.400 A
50. 0.281 H
52. 0.220 H
54. (a) 503 Hz (b) $12.0 \mu\text{C}$
(c) 37.9 mA (d) $72.0 \mu\text{J}$
56. (a) 2.51 kHz (b) 69.9Ω
60. $9t^2 / \pi^2 C$
62. (a) $-LK$ (b) $-Kt^2 / 2C$ (c) $2\sqrt{LC}$
64. (a) See solution (b) $91.2 \mu\text{H}$ (c) $90.9 \mu\text{H}$
66. (a) 127 (b) 0.522Ω (c) 76.8 mH
68. (a) 20.0 ms (b) 37.9 V
(c) 3.04 mV (d) 104 mA
70. 95.6 mH
72. (a) $I_L = 0$, $I_C = \frac{E_0}{R}$, $I_R = \frac{E_0}{R}$, $\Delta V_L = E_0$, $\Delta V_C = 0$, $\Delta V_R = E_0$
(b) $I_L = I_C = I_R = 0$, $\Delta V_L = 0$, $\Delta V_C = E_0$, $\Delta V_R = 0$
74. (a) $251 \mu\text{H}$ (b) $25.1 \mu\text{H}$ (c) 25.1 nC
76. $3.97 \times 10^{-25} \Omega$
78. (a) 50.0 mT (b) 20.0 mT
(c) 2.29 MJ (d) 318 Pa