

Chapter 33 Even Answers

2. (a) 193Ω (b) 144Ω
4. (a) 25.3 rad/s (b) 0.114 s
6. $I = 1.25 \text{ A}$ and $R = 96.0 \Omega$ for lamps 1 and 2; $I = 0.833 \text{ A}$ and $R = 144 \Omega$ for lamp 3
8. 7.03 H
10. 3.14 A
12. 3.80 J
14. (a) $f > 41.3 \text{ Hz}$ (b) $X_C < 87.5 \Omega$
16. $\sqrt{2}C(\Delta V_{\text{max}})$
18. -32.0 A
20. 2.79 kHz
22. (a) 109Ω (b) 0.367 A (c) $0.367 \text{ A}, 100 \text{ rad/s}, -51.3^\circ$
24. 1.88 V
26. See solution.
28. (a) 2.00 A (b) 160 W (c) $I_{\text{rms}}^2 R = 160 \text{ W}$
30. 353 W
32. (a) 5.43 A (b) 0.905
 (c) $281 \mu\text{F}$ (d) 109 V
34. $\sqrt{\frac{800\rho d\mathcal{P}}{\pi(\Delta V_{\text{rms}})^2}}$
36. 46.5 pF to 419 pF
38. (a) 3.56 kHz (b) 5.00 A
 (c) 22.4 (d) 2.24 kV
40. $\frac{4\pi(\Delta V_{\text{rms}})^2 RC\sqrt{LC}}{4R^2C + 9.00L}$

42. (a) 9.23 V (b) 4.55 A (c) 42.0 W
44. (a) 1600 windings (b) 30.0 A (c) 25.3 A
46. (a) 83.3 (b) 54.0 mA (c) 185 k Ω
48. (a) $\cong 1.00$ (b) 0.346
50. 8.42 Hz
56. 99.6 mH
58. (a) $\frac{\Delta V_{\max}}{R} \cos \omega t$ (b) $\frac{1}{2} \frac{(\Delta V_{\max})^2}{R}$ (c) $\frac{\Delta V_{\max} \cos \left[\omega t + \text{Arctan} \left(\frac{\omega L}{R} \right) \right]}{\sqrt{R^2 + \omega^2 L^2}}$
- (d) $C = \frac{1}{\omega_0^2 L}$ (e) R (f) $\frac{(\Delta V_{\max})^2 L}{2R^2}$
- (g) $\frac{1}{2} L \frac{(\Delta V_{\max})^2}{R^2}$ (h) $\arctan \left(\frac{3}{2R} \sqrt{\frac{L}{C}} \right)$ (i) $\frac{1}{\sqrt{2LC}}$
60. (a) 1.25 A (b) Current lags voltage by 46.7°
62. (a) 224 rad/s (b) 500 W (c) 221 rad/s and 226 rad/s
64. 58.7 Hz or 35.9 Hz
68. (a) 173 Ω (b) 8.66 V
70. See solution.